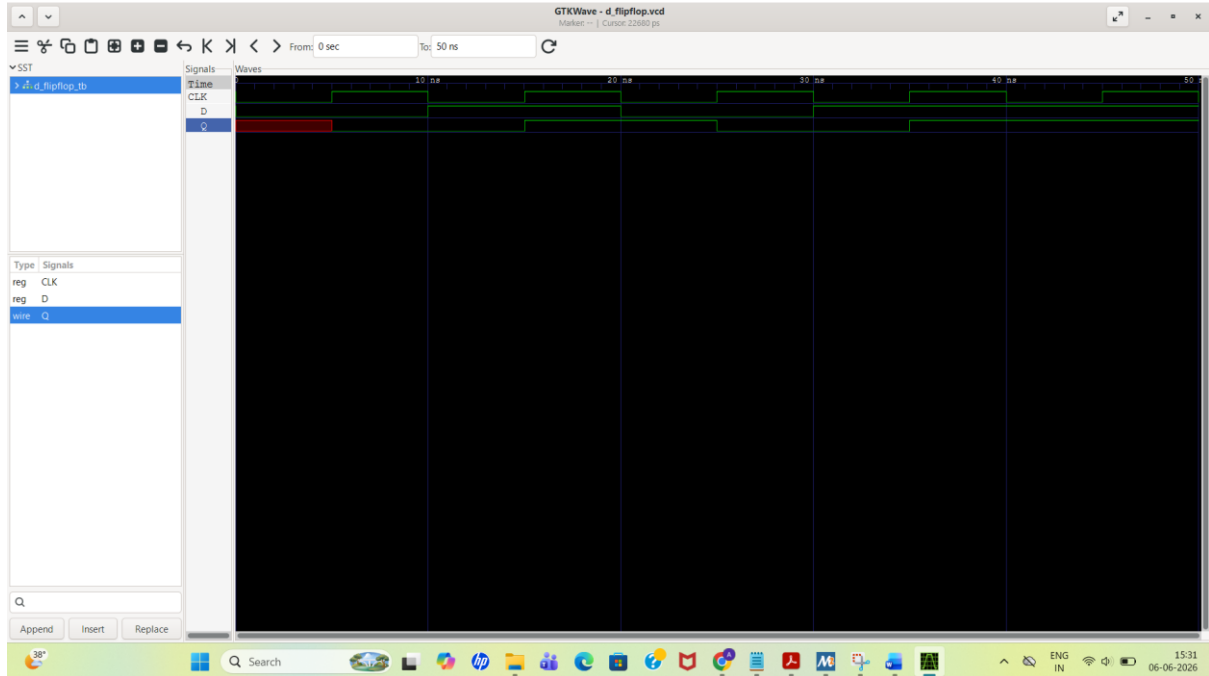



SIMULATION WAVEFORMS

TASK-3


1. D FLIP-FLOP



2. JK FLIP-FLOP

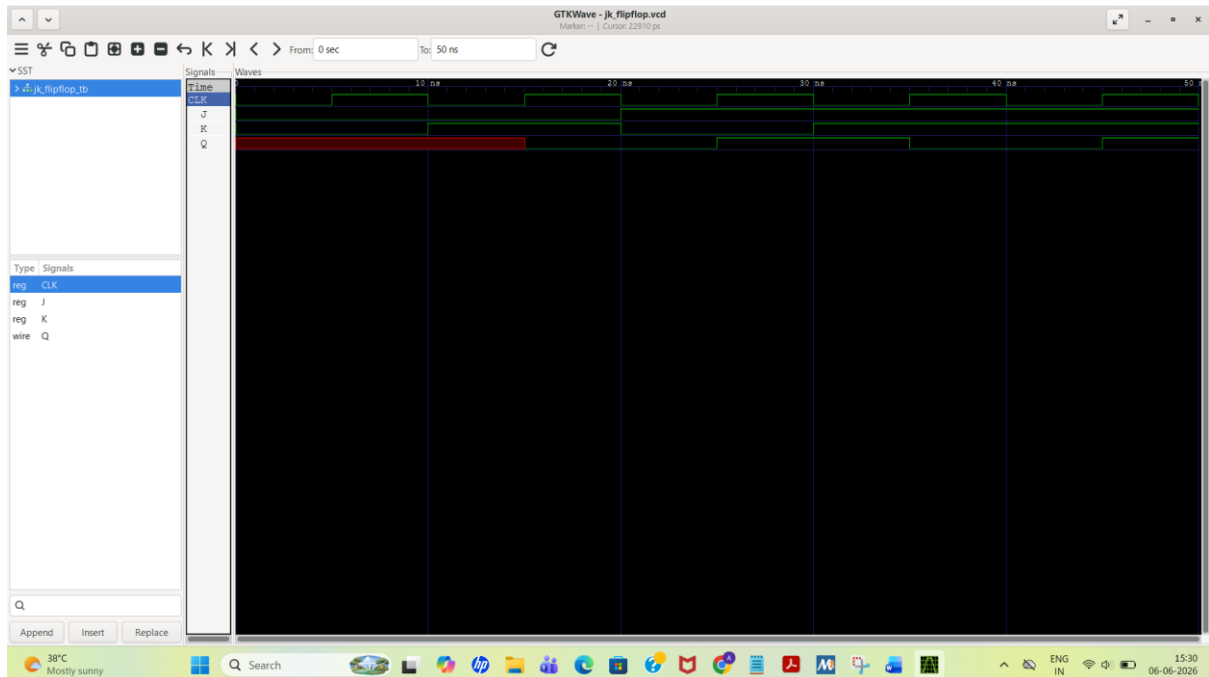

3. 4 BIT REGISTER

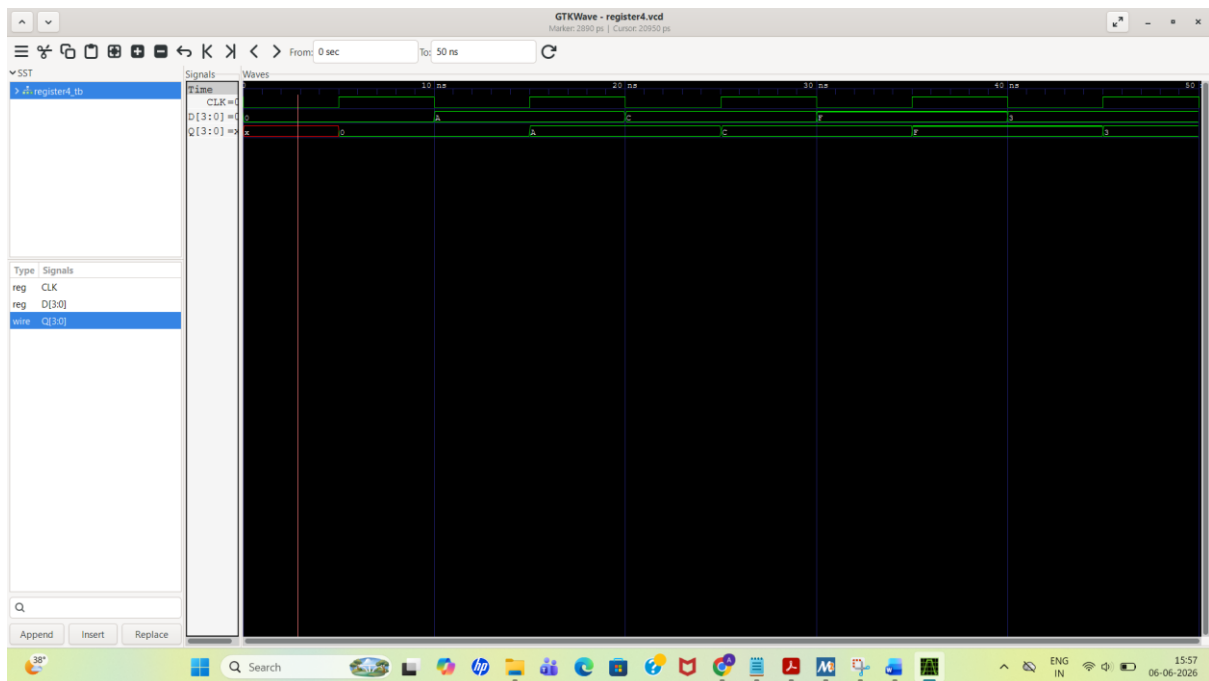

4. 4 BIT COUNTER

